

22323

11920

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

- Instructions* – (1) All Questions are *Compulsory*.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary
- (5) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.
- (6) Any calculator is not permissible.

Marks

- 1. Attempt any FIVE of the following:** **10**
- a) List one application of each of following:
- (i) Gray code
- (ii) ASCII code
- b) State the principle of multiplexer and mention its two types.
- c) Draw the circuit of one bit memory cell.
- d) List features of 8086 microprocessor. (Any four)
- e) Convert the following numbers into Hexadecimal number.
- (i) $(10110111)_2 = (?)_{16}$
- (ii) $(567)_8 = (?)_{16}$
- f) State four characteristics of RISC processor.
- g) Give example of any two types of addressing mode of 8086.

P.T.O.

2. Attempt any THREE of the following: 12

- Perform the following subtraction using 1's complement and 2's complement $(1010\ 0101)_2 - (1110\ 1110)_2$.
- Simplify the given equation into standard SOP form
 $Y = AB + A\bar{C} + BC$ and represent the same equation in standard POS form.
- Differentiate between D FF and T FF.
- Describe the characteristics of digital IC's (Any four).

3. Attempt any THREE of the following: 12

- Reduce the following boolean expression using laws of Boolean algebra and realize using basic logic gates.
 $Y = (A + BC)(B + \bar{C}A)$
- Write an assembly language program to transfer block of 10 numbers from one memory location to another. (Assume suitable data.)
- For the given circuit, identify the inputs and outputs. Name the circuit and draw its truth table. Refer Fig. No. 1.

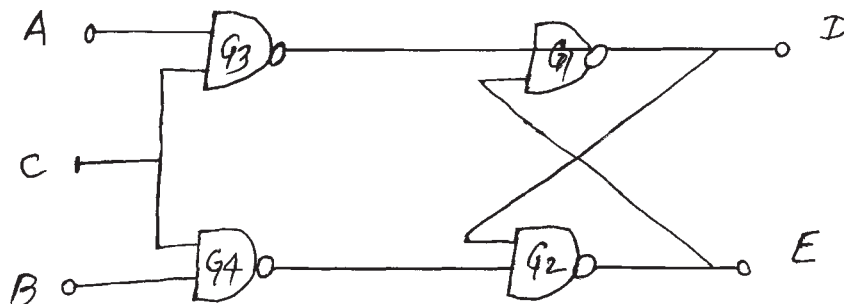


Fig. No. 1

- Simplify the given K-map using standard form and realize the circuit using gates. Refer Fig. No. 2.

		AB			
		00	01	11	10
C	0	1			1
	1		1	1	

Fig. No. 2

- 4. Attempt any THREE of the following:** **12**
- a) Write an assembly language program to find the sum of series of ten numbers stored in memory. (Assume suitable data.)
 - b) Minimize the four variable logic function using K-map.
 $f(A,B,C,D) \Sigma m (0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$
 - c) Differentiate between sequential and combinational logic circuits. (Any four points)
 - d) Describe the use of flag register and segment registers in 8086.
 - e) Describe the construction of half adder using K-map.
- 5. Attempt any TWO of the following:** **12**
- a) Write an assembly language program to find the factorial of a number using looping process.
 - b) Describe the principle of working of JK FF and draw its circuit diagram and truth table.
 - c) Differentiate between CISC and RISC and justify use of each of them in practice.
- 6. Attempt any TWO of the following:** **12**
- a) Describe the concept of pipelining and process of physical address generation in 8086 microprocessor.
 - b) State the names of universal logic gates and design basic gates using universal gates.
 - c) Describe the use of shift and rotate instructions as well as string instructions with the help of one relevant examples of each.
-